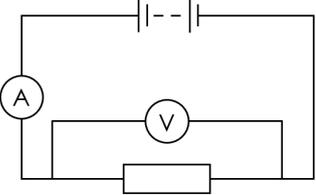
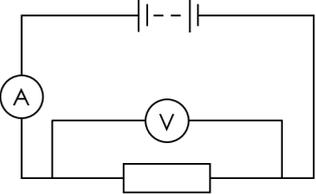
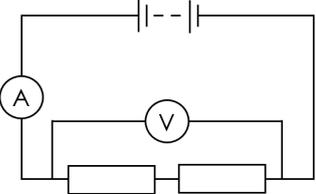


# Practical – Resistors

Circuit	Voltage / V	Current / A	Total Resistance / $\Omega$
<p>First Resistor</p> 			
<p>Second Resistor</p> 			
<p>Series</p> 			
<p>Parallel</p> 