
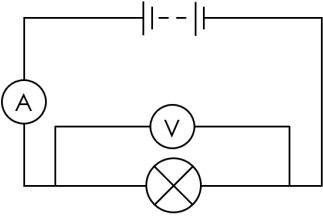
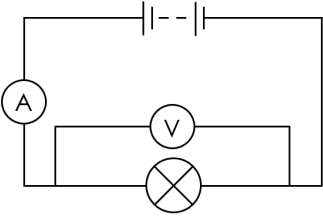
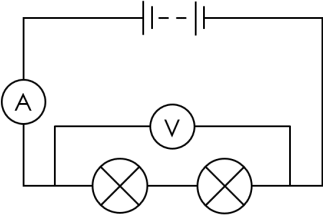


# Practical – Lamps (Filament Bulbs)

Circuit	Voltage / V	Current / A	Total Resistance / $\Omega$
First Lamp 	5.73	0.09	
Second Lamp 	5.71	0.09	
Series 	5.77	0.06	
Parallel 	5.48	0.18	

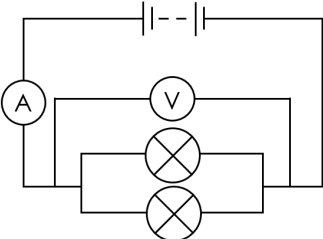