
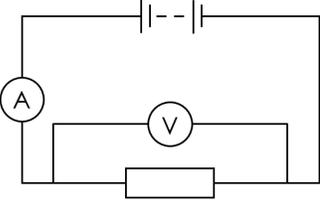
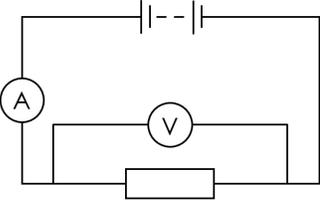
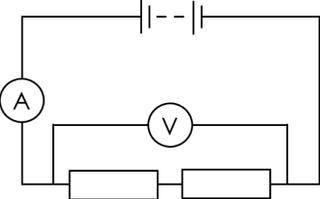


# Practical – Resistors

Circuit	Voltage / V	Current / A	Total Resistance / $\Omega$
First Resistor 	2.68	0.26	
Second Resistor 	2.67	0.25	
Series 	2.76	0.13	
Parallel 	2.46	0.47	

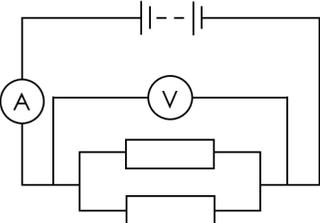